
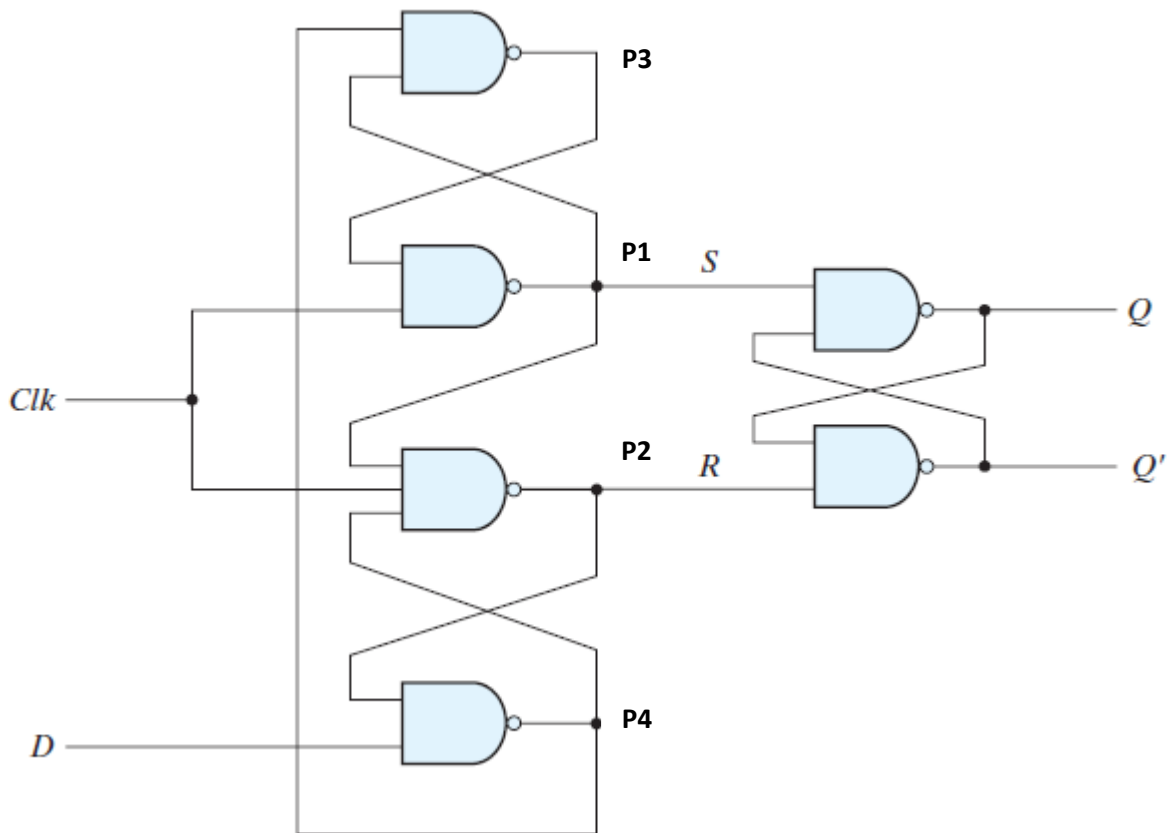


## D Flip-Flop using 6 NAND gates

Written by Asadullah Jamalov 26.04.2020

 

Above circuit is efficient design (with fewer transistors) of positive edge D flip-flop. In this report, I will introduce the working principals and the Timing Diagrams (in both ModelSim and MultiSim) of this circuit. Firstly, I would say that, this scheme consists of 3 S'R' latches.




$S$	$R$	$Q$	$Q'$
1	0	0	1
1	1	0	1
0	1	1	0
1	1	1	0
0	0	1	1

(b) Function table


Let's explain "how the above circuit works?" (look at the first picture):

- When  $\text{Clk}=0$ ,  $P1$  and  $P2$  are high ( $P1=P2=1$ ). That is why it is keeping the values of  $Q$  and  $Q'$  intact (look at the table of  $S'R'$  latch).
- Now when  $\text{Clk}=1$  (at positive edge), the values of  $P4$  (complement of  $D$ ) and  $P3$  (equal  $D$ ) pass through  $P1$  and  $P2$ .
  - Now  $P1=P4=D'$  and  $P2=P3=D$  which means  $Q=D$  and  $Q'=D'$  (look at the table of  $S'R'$  latch).
    - When  $D=0$ ,  $P2=0$  which will keep the value of  $P4=1$  regardless of the value of  $D$ .
    - When  $D=1$ ,  $P1=0$  which will keep the value of  $P2=1$  regardless of the value of  $D$ .
    - This implies that the above circuit ignores the changes in  $D$  when  $\text{Clk}=1$  after positive edge of the clock.

 Let's look at the timing diagrams of positive edge D flip-flop in ModelSim & MultiSim:



 The figure above is the timing diagram of this circuit in ModelSim Software. As seen from the graph, the value of "out" updates (according to value of "in") only in the positive edges of "clk".



Above diagram is the oscilloscope output of this circuit in MultiSim Software.